
Gate level circuit to linked list conversion

Overview

- **Benchmarking**
- **Circuit benchmark formats**
- **Input parsing**
- **Recommended data structures**
- **Circuit/Graph path counting algorithm**

Benchmarking

- Used to evaluate the performance of the developed CAD tool.
- Allows for better sharing and fair comparison of research results.
- Encourages healthy competition.
- Development of “good” benchmarks is an important research topic.

Circuit Benchmarks

- **Some of the circuit benchmarks that have been used extensively to evaluate VLSI test related research:**
 - **ISCAS'85: Combinational circuit profiles**
 - **ISCAS'89: Sequential circuits; we will use the full-scanned versions**
 - **ITC'99: The most recent and most challenging!**


ISCAS: International Symposium of Circuits And Systems

ITC: International Test Conference

ISCAS'85/ISCAS'89/ITC'99 Bench Format

Header	# c17 # 5 inputs # 2 outputs # 0 inverter # 6 gates (6 NANDs)
Primary Inputs	INPUT(1) INPUT(2) INPUT(3) INPUT(6) INPUT(7)
Primary Outputs	OUTPUT(22) OUTPUT(23)
Gates	10 = NAND(1, 3) 11 = NAND(3, 6) 16 = NAND(2, 11) 19 = NAND(11, 7) 22 = NAND(10, 16) 23 = NAND(16, 19)

Circuit c17 from the ISCAS'85 suite

 

ISCAS'85/ISCAS'89/ITC'99 Bench Format

- **keyword**
- **variable**
- **#** - comment line
- **INPUT(x)** - primary input line with name **x**
- **OUTPUT(x)** - primary output line with name **x**
- **x = GTYPE(IN1, IN2, ..., INk)** - gate of type **GTYPE** with output **x** and **k** inputs, **IN1...INk**
- Valid gate type **GTYPE**
AND, NAND, OR, NOR, XOR, XNOR, NOT, BUFF

Parse bench circuit and store as graph


c17
5 inputs
2 outputs
0 inverter
6 gates (6 NANDs)

INPUT(1)
INPUT(2)
INPUT(3)
INPUT(6)
INPUT(7)



OUTPUT(22)
OUTPUT(23)

10 = NAND(1, 3)
11 = NAND(3, 6)
16 = NAND(2, 11)
19 = NAND(11, 7)
22 = NAND(10, 16)
23 = NAND(16, 19)


Circuit c17 from the ISCAS'85 set

 

  Recommended data structures (example for circuit c17)



1D array with linked lists

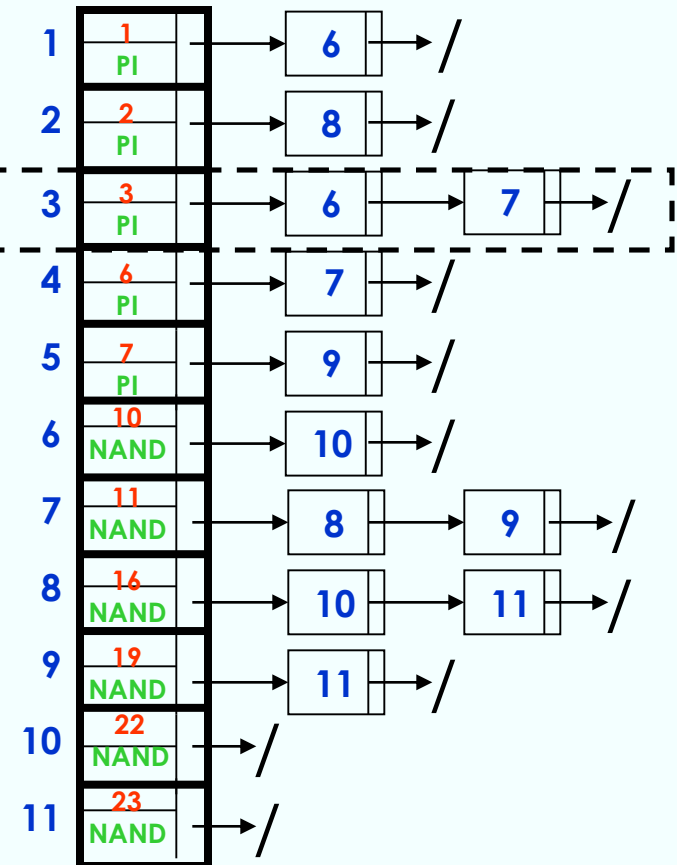

Adding BRANCH nodes to the graph



- The bench format does not *explicitly* define fanout stems and branches

- It is implied that:




$x = \text{AND}(a, b, c)$

$y = \text{NOT}(a)$



$z = \text{OR}(a, b)$

  

   - To add branch nodes to the graph, define a new node type **BRNH**, and:



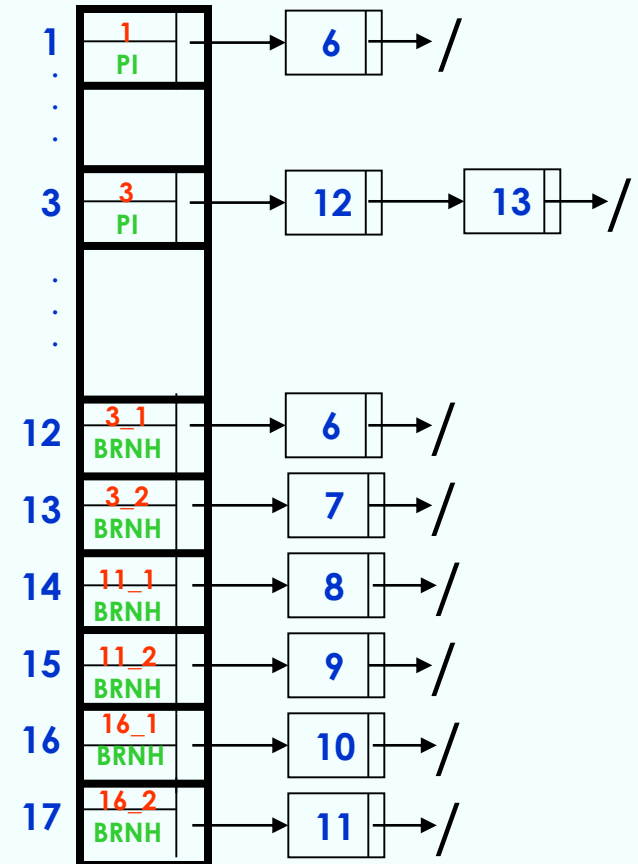 Adding BRANCH nodes to the graph (example for circuit c17)



Circuit/Graph Path Counting

- Problem of counting the # of paths in a combinational circuit reduces to a *modified* topological traversal.
- Let node v with $S(v)$ = set of immediate predecessors of v . The # of paths up to v , defined by $p(v)$, is:

$$p(v) = \sum p(i), i \in S(v)$$

Graph Path Counting Algorithm

Input: $G(V,E)$ with PI = set of nodes with no predecessors, PO = set of nodes with no successors, and $S(v)$ = set of immediate successors of node v .

Output: # of paths in G

Algorithm Count_Paths(G)

Step 1: FOR (every $v \in V$)

 IF ($v \in PI$) $p[v] = 1$; mark v as visited;

 ELSE $p[v] = 0$; mark v as not-visited;

Step 2: Run topological traversal algorithm; modified such that when a node v is processed, calculate $p(v) = \sum p(i), i \in S(v)$

Step 3: Return $\sum p(v), v \in PO$